

CS 250 Spring 2017 - Lab 03

Due in lab Feb. 07-10, 2017

Submit your typewritten file in PDF format to Blackboard

Questions

1. [15 points; 5 points for each for result] Does the timing of the 555 clock output match the predictions of the equations for frequency, t_{high} , and t_{low} that are given below the schematic? Show a calculation of the expected value for each of the three parameters..

$$\text{Frequency} = 1/(\ln(2) * C2 * (R1 + 2 * R2)) = \\ = 1 / (\ln(2) * 0.001F * (470\Omega + 2 * 470\Omega)) = \mathbf{1.023 \text{ Hz}}$$

$$t_{\text{high}} = \ln(2) * (R1 + R2) * C2 \\ = \ln(2) * (470\Omega + 470\Omega) * 0.001F = \mathbf{0.6516 \text{ seconds}}$$

$$t_{\text{low}} = \ln(2) * R2 * C2 \\ = \ln(2) * 470\Omega * 0.001F = \mathbf{0.3258 \text{ seconds}}$$

2. [10 points] The 74HC163 is a 4-bit counter, but this lab needs only a 3-bit counter. How can you obtain a 3-bit counter from the output of a 4-bit counter? Which three of the output signals would you select and why?

You can obtain a 3-bit counter from the output of a 4-bit counter by simply excluding the most significant bit. We would select the three output signals of the three least significant bits. This works because in a 4-bit sequence the 3 least significant bits just repeat (if ignoring the most significant bit), thus acting like a 3-bit counter.

3. Derive the Boolean expressions for each color of the stoplight, and simplify in terms of 2-input NAND and NOR gates. Show your work to earn credit. Your Boolean expression must be in terms of QA, QB, QC, and QD, for the counter outputs, and/or D0 – D7 for the eight decoder/demux outputs. Draw the final schematic diagram using NAND and NOR gates for each color.

- a. [10 points] Green light Boolean expression and schematic.

Qc	Qb	Qa	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


Qc Qb

Qa

	00	01	11	10
0	1	1	0	0
1	1	0	0	0

K-Map: $Qc'Qb' + Qc'Qa'$

NAND: $((Qc'Qb')' * (Qc'Qa'))'$

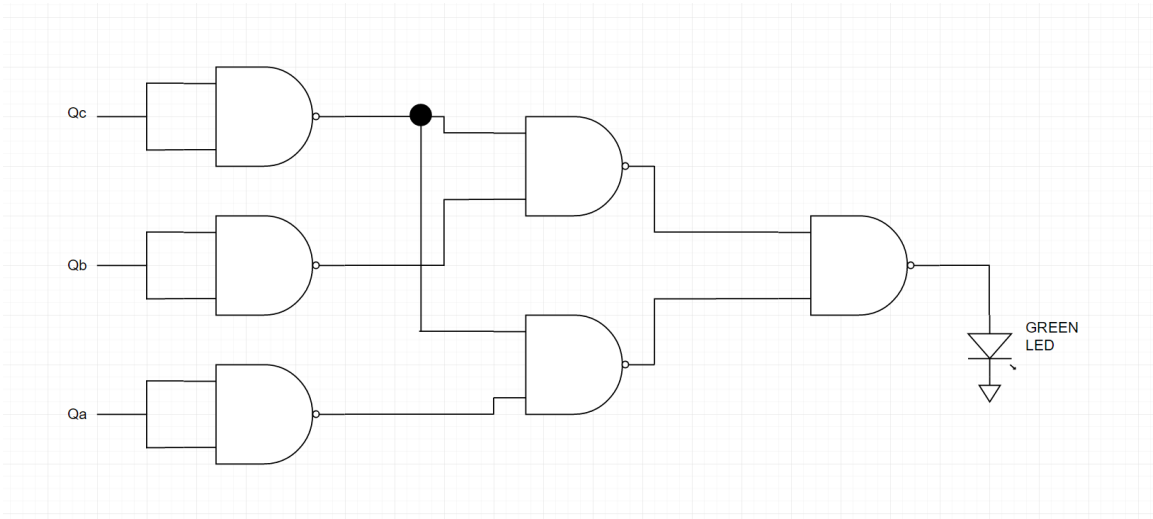


b. [10 points] Yellow light Boolean expression and schematic.

Qc	Qb	Qa	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

~~Qc Qb~~

	00	01	11	10
0	0	0	0	0
1	0	1	0	0

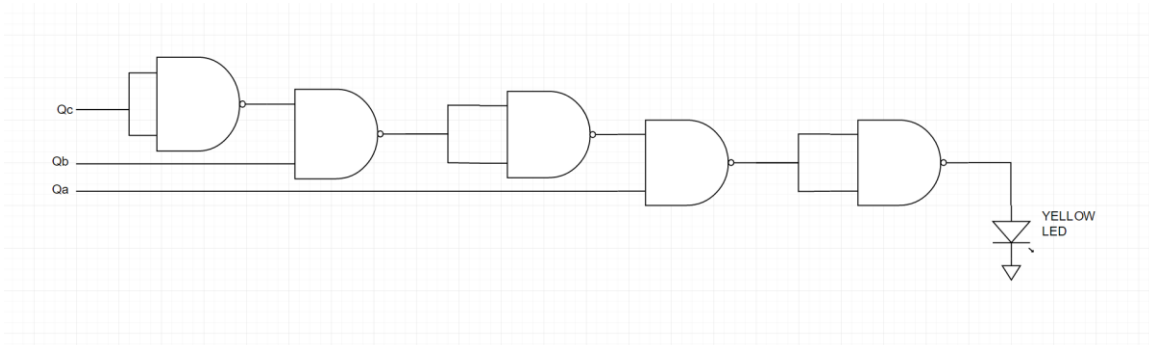


c. [10 points] Red light Boolean expression and schematic drawing of gates.

Qc	Qb	Qa	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Qc Qb

Qa

	00	01	11	10
0	0	0	1	1
1	0	0	1	1

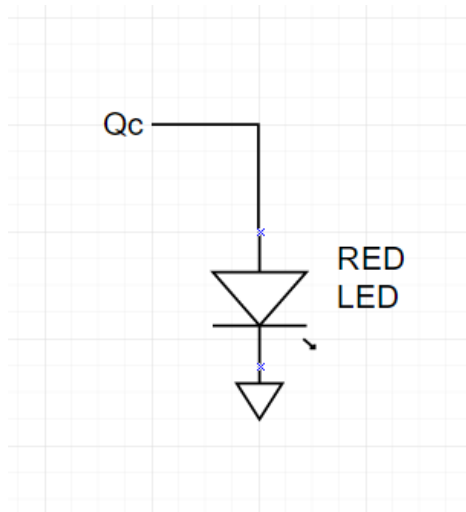

4. Demonstrate your circuit to your TA. Full credit when the order and timing of lights is correct.
 - a. [15 points] Green light turns on for 3 seconds, then
 - b. [15 points] Yellow light turns on for 1 second, then
 - c. [15 points] Red light turns on for 4 seconds.